 


$$F_1 = \underline{\bar{B}\bar{C}} + \underline{\bar{A}\bar{C}} + \bar{A}\bar{B}$$

$$F_2 = \underline{\bar{B}\bar{C}} + \underline{\bar{A}\bar{C}} + ABC$$



((PLA Logic cct))


Synchronous Sequential Logic Circuits:-

Up to now everything has been combinational, that is the o/p at any instant of time depends only on what the i/p's are at that time. (This ignores the small delay between the time the input of circuit changes and when the o/p changes).

A sequential system:- It is a system that has memory, thus, that output will depend not only on the present i/p but also on the past history what has happened earlier. We will deal almost with clocked systems (sometimes referred to as synchronous).

A clock is just a signal that alternates (over time) between 0 and 1 at a regular rate. In the figure below, the clock signal is 0 half of the time and 1 half of the time.

 
The period of the signal (T on the diagram) is the length of one cycle. The frequency is the inverse ($1/T$).



clocked sequential circuits are the type most frequently encountered in practice.

The storage elements used in clocked sequential ccts are called Flip - Flops .

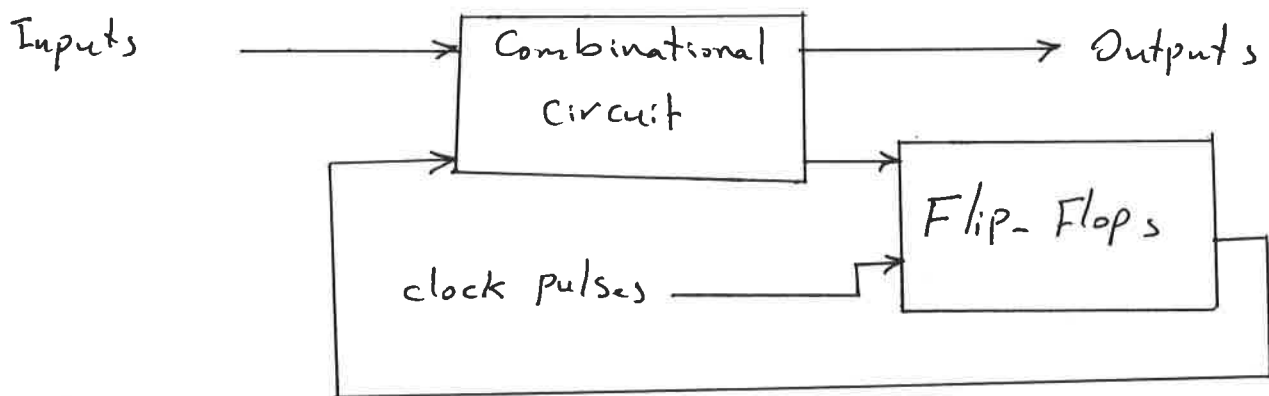A Flip-Flops is a binary storage device capable of storing one bit of information . A sequential circuit may use many F.F's to store as many bits as necessary . The block Diagram of a synchronous clocked sequential system is shown belows .



Latches :- It is the most basic types of Flip-Flops operate with signal levels. The latches are the basic circuits from which all Flip-flops are constructed . Although latches are useful for storing binary information and for the design of asynchronous sequential circuits .

A flip-flop is a clocked binary storage device, that is, a device that stores either a 0 or 1 . Under normal operation, the value will only change on the appropriate transition of the clock . The state of the system (what is in memory) changes on the transition of the clock . For some flip-flops, that change

take place when the clock goes from 1 to 0; that is referred to as trailing-edge triggered. For others that changes takes place when the clock goes from 0 to 1; that is referred to as leading edge triggered. Figures below show that.

- In general a combinational system,

- 1- No feed back to the system from the output.
- 2- No memory required.

- In general sequential system,

- 1- There is feedback to the input from output.
- 2- It has a memory.

Flip-Flops :-

It is a cct that maintain a binary state until directed by an I/P signal, to switch state. The major difference between different types of flip-flop are:-

- 1- No. of I/P's they have.
- 2- The manner in which the i/p's effects the Binary state.

The .F.F find wide application in Digital system such as :-

- 1- Counters.
- 2- Registers.
- 3- Memory.
- 4- control Logic.

Types of Flip-Flops:-

- 1- (S-R) Set-Reset Flip-Flop.
- 2- (J-K) Flip-Flop.
- 3- T (Toggle) Flip-Flop.
- 4- D (Delay) Flip-Flop.

D) (SR - F/F) (Set-Reset F.F) :-


The F.F has 2 stable state. It is capable of being on either a "high" state (Logic 1) or a "Low" state (Logic 0).

2 states are Set & Reset

Set: Q output is Logic 1 Set
 Q' output is Logic 0


Reset: Q output is Logic 0 Reset
 Q' output is Logic 1

 and S-R (Set-Reset) is formed with 2-cross-coupled NAND gates or 2-NOR gates



The o/p of NOR gate is (0) if any I/P is (1) and the o/p is (1) only when all inputs are (0).

The block Diagram of SR/F.F is :-

 


Block Diagram of (S-R)/F.F

The truth table of SR/F.F is :-


S	R	Q
0	0	Last case (No. change)
0	1	0 Reset
1	0	1 Set
1	1	X Forbidden (Not allowed)

Bubbled and Gate :-

 
We can change the NOR gate to bubbled gate according to De-morgan's Theorem.



 ② Bubbled OR :- We can change the NAND gate by bubbled gate such as:-



 We can get SR/F.F from the (NAND) gates as shown below:-



S	R	Q_n	Q_{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	1	0	X
1	1	1	X

* Q_n i/p
 * Q_{n+1} next output

We can simplified the truth table to:-

S	R	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	X

The ch/s eq. of RS Flip-Flop is:-

$$Q_{n+1} = S + \bar{R}Q_n$$

$Q_n \backslash SR$	00	01	11	10
0	0	0	X	1
1	1	0	X	1

There is another useful table called "Excitation table"

S	R	Q_n	Q_{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	X
1	1	1	X

Q_n	Q_{n+1}	S	R
0	0	0	d
0	1	d	0
1	0	0	1
1	1	1	0


* d dont care

* 0 means SR are both are (1)


not allowed, or both (1) in SR do not allowed.

The clock SR/F.F

 
We can use the pulses (synchronous pulses) in Digital systems to operate this system with clock, we can shown the clock pulse :-



 When:- $(Cp=0)$ no change
 $(Cp=1)$ Apply (SR)





The clock SR/F.F

 

Cp	S	R	Q_{n+1}
0	0	0	} No change
0	0	1	
0	1	0	
0	1	1	
1	0	0	no change
1	0	1	0
1	1	0	1
1	1	1	X

D Flip-Flop :-

  
It is the most economical and efficient Flip-Flop constructed. Because it required the smallest number of gates. The name comes from Delay, since the o/p is just the i/p delayed until the next active clock transition. Block Diagram of D/F.F is shown below :-



The truth table:-

D	Q_{n+1}
0	0
1	1

 We can use the SR/F.F to build the D/F.F., use the (NAND) gate as Not to prevent (1, 1).



When:- (D=0), $S=0$, $R=1$, $Q_{n+1}=0$

(D=1), $S=1$, $R=0$, $Q_{n+1}=1$

* As the (S) and (R), one reverse the other, so the (D=1), make the F.F in (Setting),

* If the (D=0), make the F.F in (Resetting), & the S, R can not be 1 for any case.