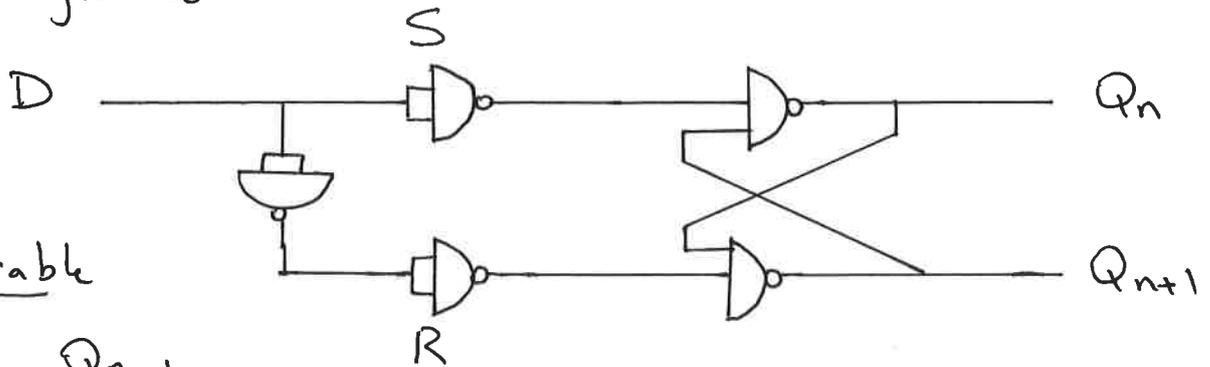


The Logic cet:-



ch/s table

$Q_n$	D	$Q_{n+1}$
0	0	0
0	1	1
1	0	0
1	1	1

$Q_n \backslash D$	0	1
0	0	1
1	2	1

$Q_{n+1} = D$  ch/s eq

T Flip-Flop :-

The trigger F.F has one input, T, such that if  $T=1$ , the F.F changes state (that is, trigger), and if  $T=0$ , the state remains the same.

The truth table of the T/F.F can shown below:-



I/P T	present $Q_n$	T/F.F next $Q_{n+1}$
0	0	0
0	1	1
1	0	1
1	1	0

\* This means  $(Q_{n+1}) = Q_n$  when  $T=0$

\*  $(Q_{n+1}) = \bar{Q}_n$ , when  $T=1$

$Q_{n+1} = T \oplus Q_n$

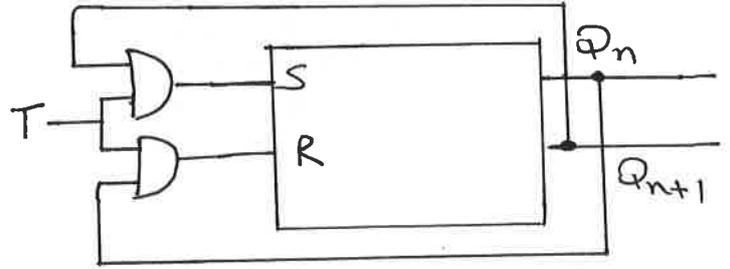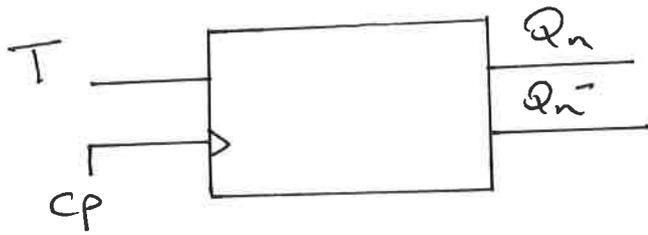The Block Diagram and the cct Diagram of T/F.F is:-



if



T	Q <sub>n</sub>	Q <sub>n+1</sub>
1	0	1

set(1)

T	Q <sub>n</sub>	Q <sub>n+1</sub>
1	1	0
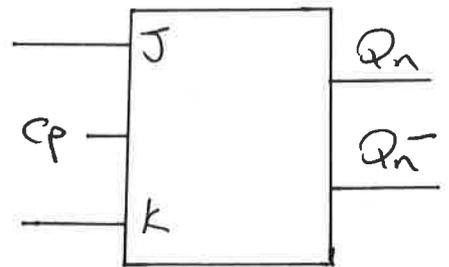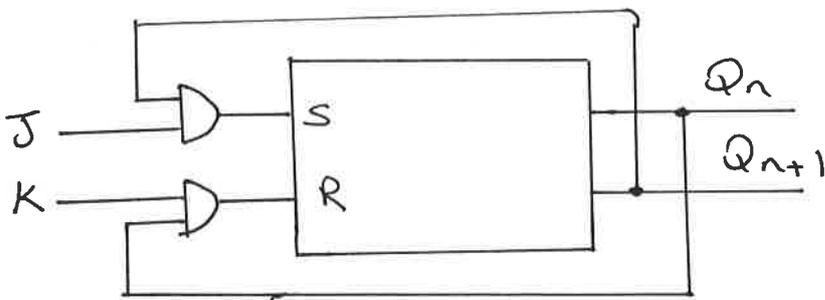
### J-K Flip-Flop:-

It is the most commonly used type of F.F. It is very similar to SR/F.F except that J.K/F.F allow to used Logic 1 on both inputs J & K, the cct Diagram of J.K/F.F is shown below:-



And the truth table of this type is shown below:-

input		Present state ( $Q_n$ )	Next state ( $Q_{n+1}$ )
J	K		
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

This table can be put in another form such that:-


J	K	$Q_{n+1}$
0	0	$Q_n$
0	1	0
1	0	1
1	1	$\bar{Q}_n$

From the set Diagram, we can conclude that:-

$$S = J \bar{Q}_n, \quad R = K Q_n$$

The ch/s equation of JK/F.F can be:-

$$Q_{n+1} = J \bar{Q}_n + \bar{K} Q_n$$

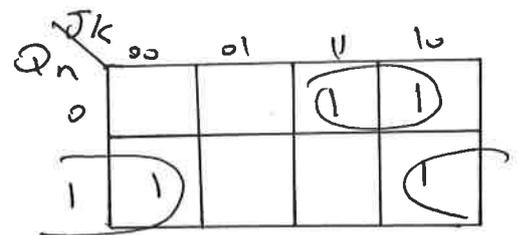


### J-K master-slave F/F :-

A master-slave F.F is a combination of 2 clocked F.F J.K or S-R/F.F.

The first is called "The master" and the second "The slave" notes that the master is positively clocked but the slave is negative.

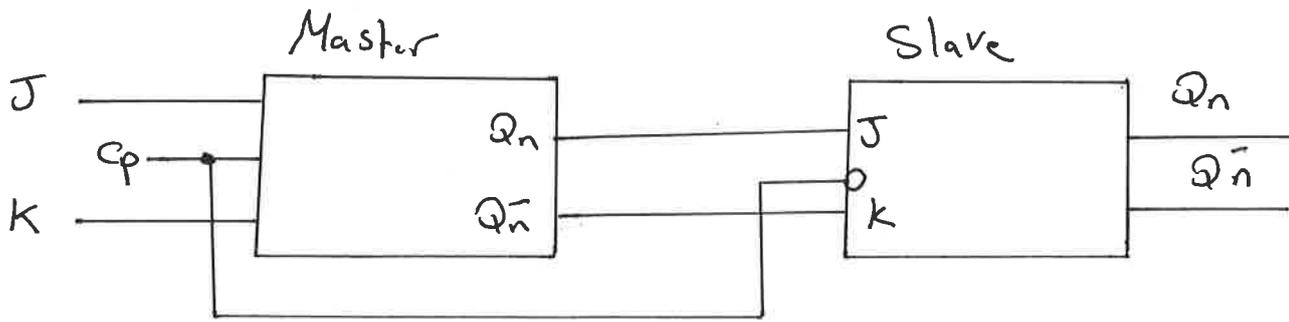The Block Diagram of such Flip-Flop is shown below



Flip-Flop Excitation table:-

The tables of the four standard Flip-Flops can be

summarized as:-

\* S-R / F.F

S	R	$Q_{n+1}$
0	0	$Q_n$
0	1	0
1	0	1
1	1	X

\* J-K / F.F

J	K	$Q_{n+1}$
0	0	$Q_n$
0	1	0
1	0	1
1	1	$Q_n$

\* D / F.F

D	$Q_{n+1}$
0	0
1	1

\* T/F.F

T	$Q_n$	$Q_{n+1}$
0	0	0
0	1	1
1	0	1
1	1	0

The Excitation table of the same F/F gives the relation between  $Q_n$  and  $Q_{n+1}$  as input and the standard i/p as o/p.


$Q_n$	$Q_{n+1}$	S	R	J	K	D	T
0	0	0	d	0	d	0	0
0	1	1	0	1	d	1	1
1	0	0	1	d	1	0	1
1	1	d	0	d	0	1	0

A synchronous inputs:-

The S-R inputs or (J-K) are called synchronous i/p's since they only effect the state of the F.F when the clock pulse is present. Some F.F have either i/p's called preset or set and clear or reset that can be used for setting F.F to Logic 1 or resetting to Logic zero, by applying the proper signal to the preset and clear inputs.

These inputs can change the state of the F.F regardless of the synchronous i/p of the block.


The Block Diagram is :-

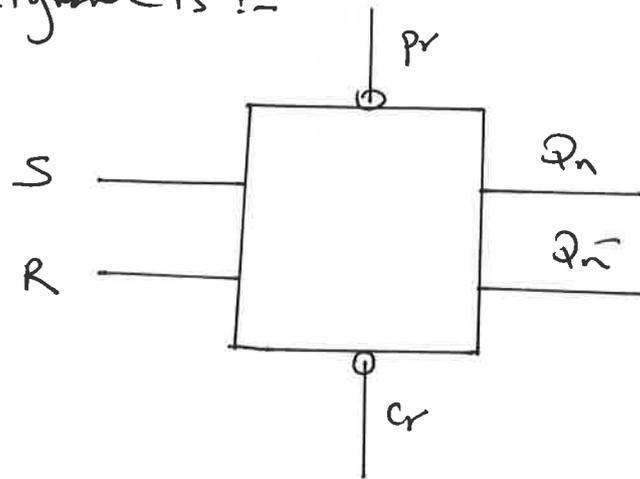

The ( $P_r$  and  $C_r$ ) can be used to determine the primary state of the Flip-Flops or/for we can setting the F.F at a certain value, regardless of input values of ( $S, R, J, K$ ), and can put the table as:-

$C_r$	$P_r$	Condition ( $Q_n$ )
0	0	Don't use
0	1	0
1	0	1
1	1	Normal condition

The Logic cct:-

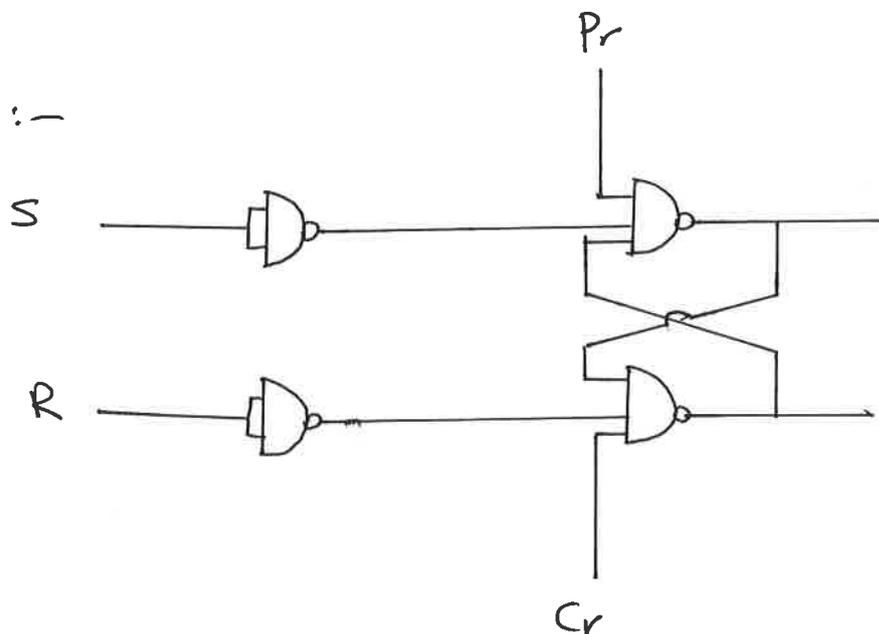


### Transformation of Flip-Flops:-

\* Transform T/F.F to J-K/F.F


\* Truth table of J-K/F.F

J	K	$Q_n$	$Q_{n+1}$	T
0	0	0	0	0
0	0	1	1	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	1
1	0	1	1	0
1	1	0	1	1
1	1	1	0	1

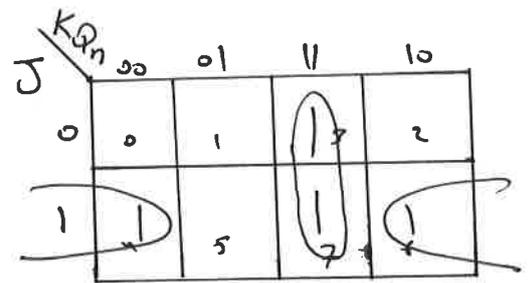

\* ch/s eq.  $T = KQ_n + JQ_n$

\* The Logic cct:-

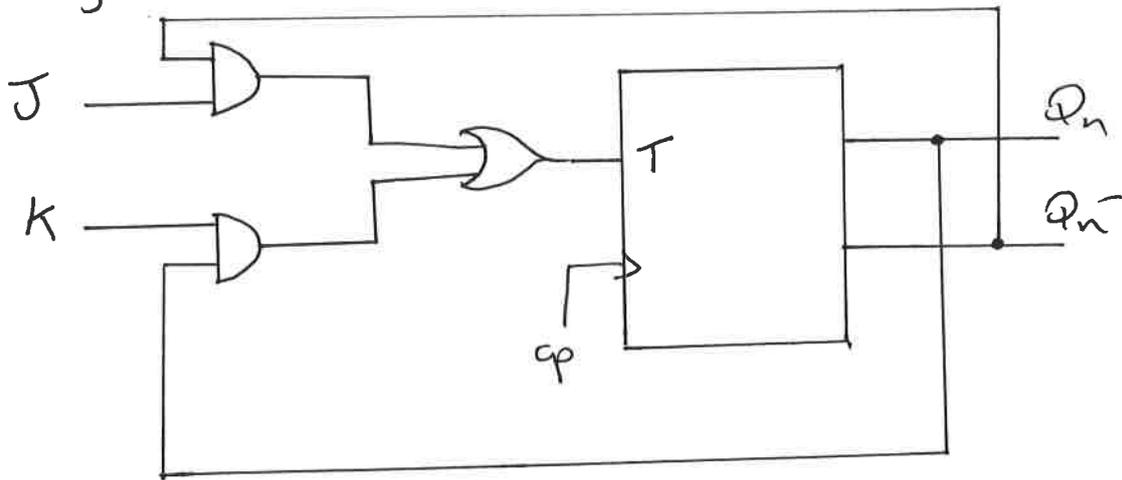


Ex) Transform T/F.F to D/F.F

D	$Q_n$	$Q_{n+1}$	T
0	0	0	0
0	1	0	1
1	0	1	1
1	1	1	0

$Q_n \backslash D$	0	1
0		1
1	1	

chls eq  $T = \bar{D}Q_n + DQ_n^-$   
 $= D \oplus Q_n$

Logic ckt:-

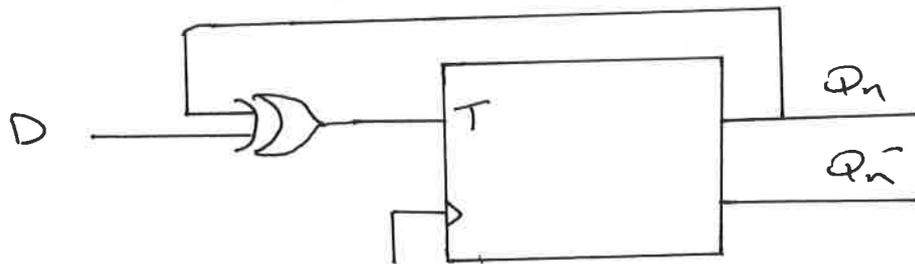


Ex) Transform D/F.F to T/F.F

T	$Q_n$	$Q_{n+1}$	D
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	0

$Q_n \backslash T$	0	1
0		1
1	1	

$D = \bar{T}Q_n + TQ_n^-$   
 $= T \oplus Q_n$

Logic ckt:-

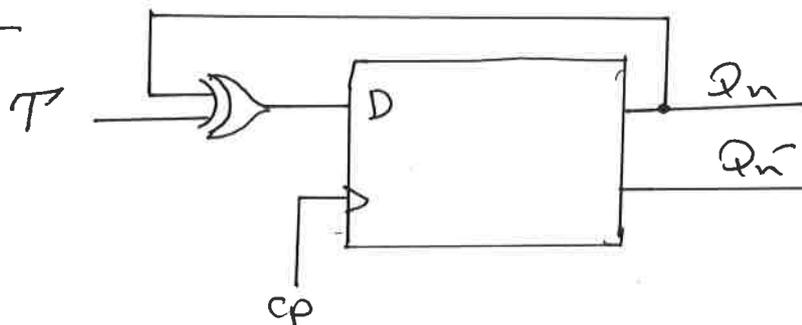

Ex) Convert S-R/F.F to D/F.F


D	$Q_n$	$Q_{n+1}$	S	R
0	0	0	0	d
0	1	0	0	1
1	0	1	1	0
1	1	1	d	0

$Q_n$	D	0	1
0	0	0	1
1	0	0	d

$S = D$

$Q_n$	D	0	1
0	d	0	0
1	1	0	0

$R = \bar{D}$

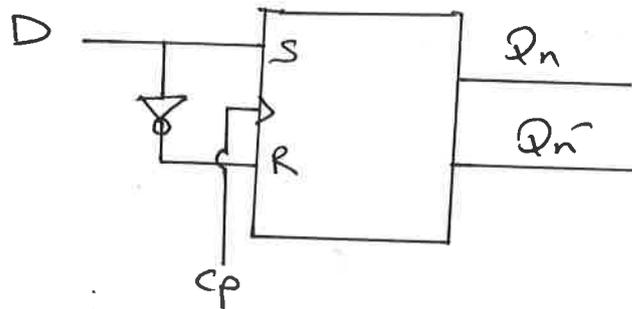

Ex) Design T/F.F by using S-R/F.F?

T	$Q_n$	$Q_{n+1}$	S	R
0	0	0	0	d
0	1	1	d	0
1	0	1	1	0
1	1	0	0	1

$Q_n$	T	0	1
0	0	0	1
1	d	d	0

$S = TQ_n$

$Q_n$	T	0	1
0	d	0	0
1	0	0	1

$R = TQ_n$

