

①

$$M \dot{X} = F$$

$M \dot{X}$

$$F = -kx$$

$$M \ddot{x} = -kx$$

$$x = Y$$

$$\omega^2 = \frac{k}{M}$$

$$x = \mathcal{R}$$

$$y = -\omega^2 x$$

$$x = \mathcal{R}$$

$$y = -\frac{kx}{M}$$

$$F = -\frac{dV}{dx}$$

2)

$V = \text{potentielle}$

$$V = \frac{1}{2} k x^2$$

$$F = -dV$$

$$F = -kx$$

$$M \ddot{x} + \frac{dV}{dx} = 0$$




$x(0) = 0$

$y(0) = 1$

$x(E) = 1 \text{ symmet}$

$y(t) = \cos t$

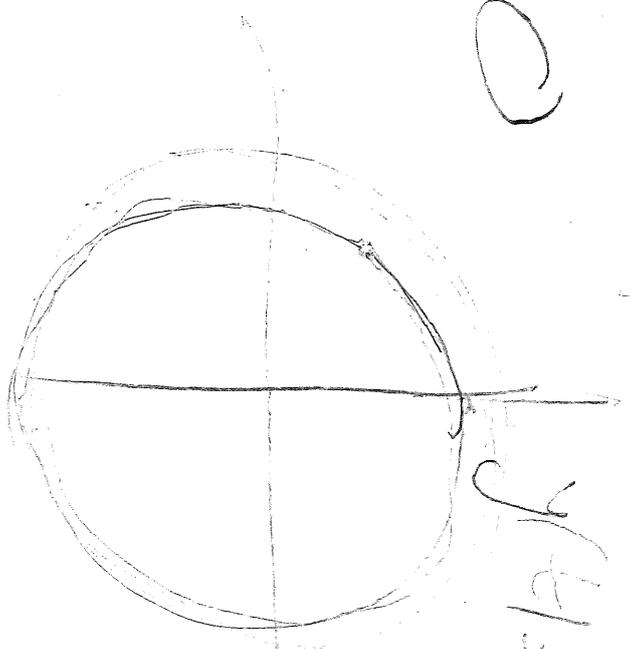

3

$$m\ddot{x} + \delta \dot{x} + \omega^2 x = F \sin(\Omega t)$$

$$\left\{ \begin{array}{l} z = \Omega t \\ \Omega \end{array} \right.$$



$$\begin{array}{l} \circ \\ \circ \\ x \end{array}$$

$$z = \Omega t$$

$$y =$$

$$z = \Omega t$$

ANALOG / DIGITAL

$$\frac{V_{in}}{CR} = -V_{out} j\omega$$

$$\frac{V_{in}(t)}{RC} = -V_{out}$$

$$V_{out} = -\frac{V_{in}}{RC} = -\delta V_{in}$$

$$RE = \tau \quad \delta = +\frac{1}{RC}$$

$$V_{out} = -\frac{1}{\delta} V_{out}$$


$$X = -\frac{1}{\delta} X$$

(11)

~~$X(t) = X_0 e^{j\omega t}$~~   
 ~~$X(t) = X_0 e^{-j\omega t}$~~

(11)  
 $\psi_t$

5

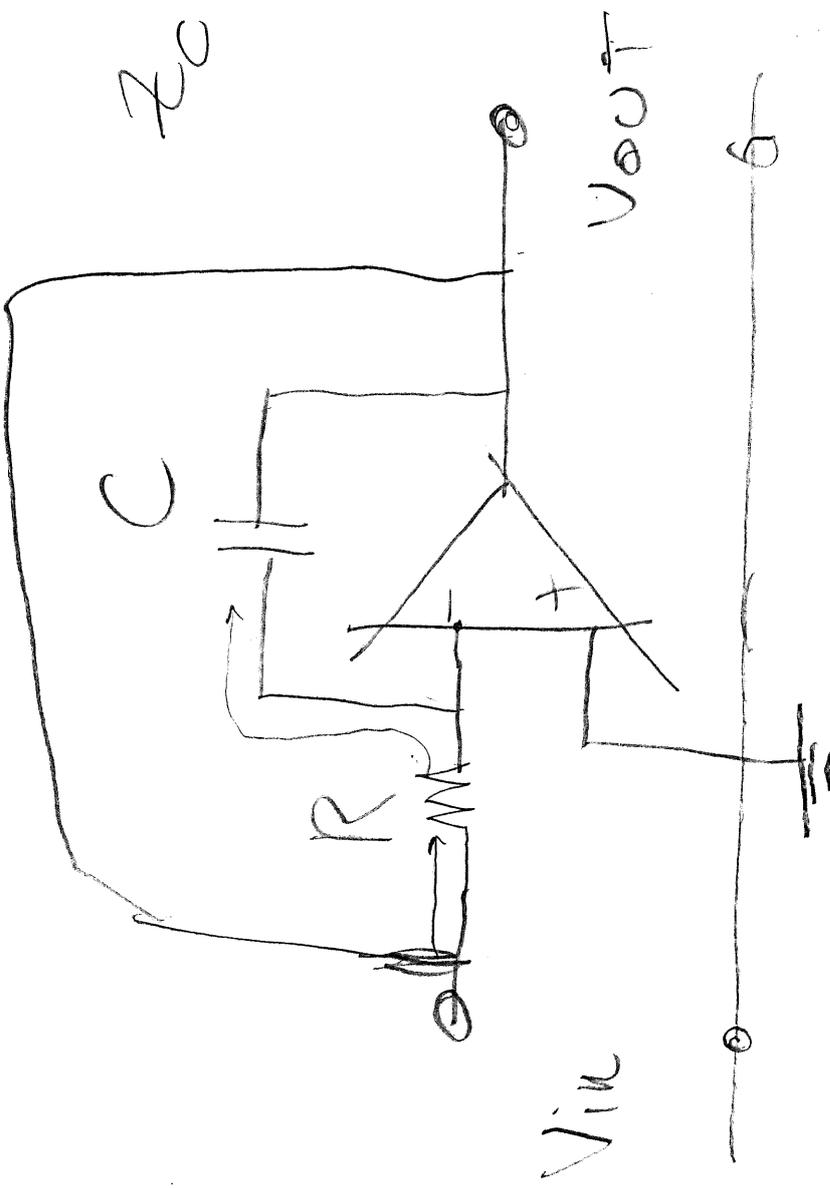


$$Z_C = \frac{1}{j\omega C}$$

$$\frac{V_{out}}{V_{in}} = -\frac{Z_C}{R}$$

$$i = \frac{V_{in}}{R} \quad i = \frac{V_{out}}{R} = \frac{1}{j\omega C}$$


$$\frac{V_{in}}{R} = -V_{out} j\omega C$$

6

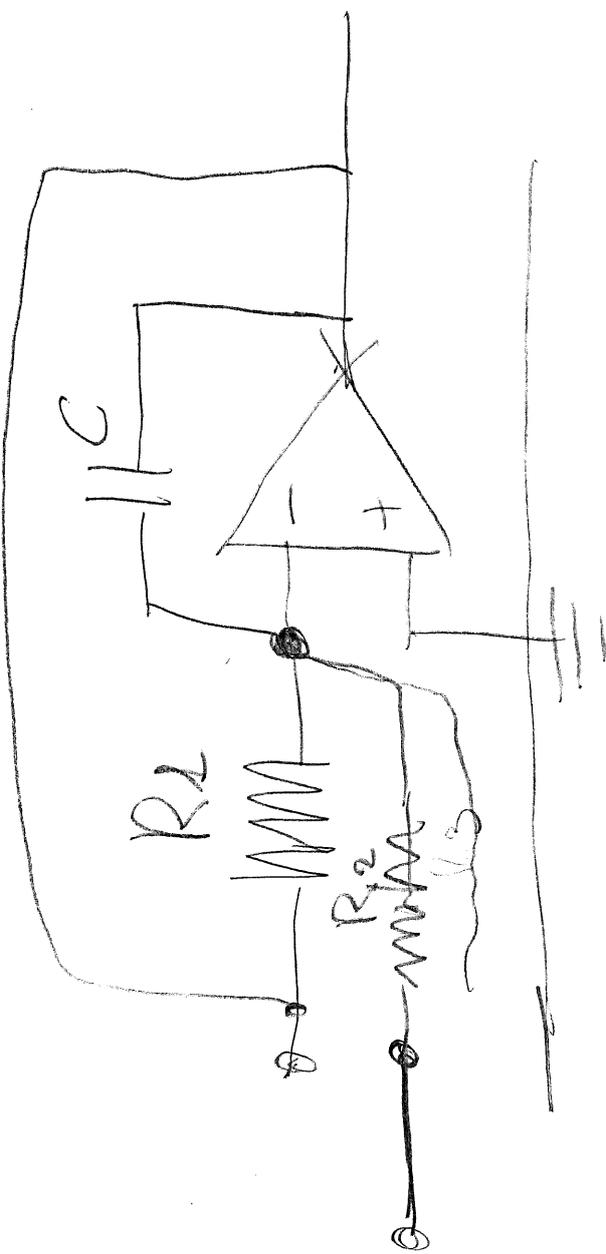

$$X = -\frac{1}{R_1 C} + \frac{1}{R_2 C} + \frac{1}{R_3 C}$$

~~Handwritten scribble~~

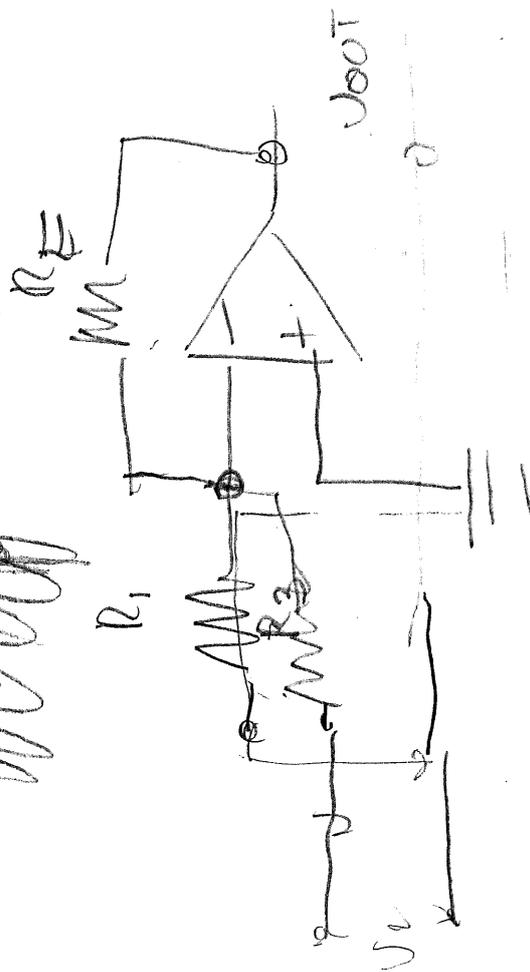

$$V_{out} = -\frac{R_F}{R_1} V_1 - \frac{R_F}{R_2} V_2$$